


FPGA 系統設計實務

期中報告

M11102150

劉家瑜

Design

 


		regEn	regSel	regData	reg 外	readA	readB	outB_in	outImm	LHI	add/sub	logicm	memread	memEn	memAddr	memData	done	pcen	pcext	pc-inc-inc
00001	LHI	1	instr[10:8]	ALUout	0	instr[10:8]		instr[7:0]	1	1	0	1	0	0	x	x	0		1	0
00010	LL1	1	instr[10:8]	ALUout	0	x		instr[7:0]	1	0	0	1	0	0	x	x	0		1	0
00011	LDR	1	instr[10:8]	MEMout	1	instr[7:5]		instr[4:0]	1	0	0	0	1	0	ALUout	x	0		1	0
00101	STR	0	x	x	0	instr[7:5]	instr[10:8]	instr[4:0]	1	0	0	0	0	1	ALUout	RB	0		1	0
00000	ADD	1	instr[10:8]	ALUout	0	instr[7:5]	instr[4:2]		0	0	0	0	0	0	x	x	0		1	0
00000	ADC	1	instr[10:8]	ALUout	0	instr[7:5]	instr[4:2]		0	0	0	0	0	0	x	x	0		1	0
00000	SUB	1	instr[10:8]	ALUout	0	instr[7:5]	instr[4:2]		0	0	1	0	0	0	x	x	0		1	0
00000	SEB	1	instr[10:8]	ALUout	0	instr[7:5]			0	0	1	0	0	0	x	x	0		1	0
00110	CMP	0	x	x	0	instr[7:5]	instr[4:2]		0	0	1	0	0	0	x	x	0		1	0
00111	ADDI	1	instr[10:8]	ALUout	0	instr[7:5]		instr[4:0]	1	0	0	0	0	0	x	x	0		1	0
01000	SUBI	1	instr[10:8]	ALUout	0	instr[7:5]		instr[4:0]	1	0	1	0	0	0	x	x	0		1	0
01011	MOV	1	instr[10:8]	ALUout	0	instr[7:5]		instr[4:0]	1	0	0	0	0	0	x	x	0		1	0
C3	BCC	0	x	x	0	x	x		0	0	0	0	0	0	x	x	0		disp	0
C2	BCS	0	x	x	0	x	x		0	0	0	0	0	0	x	x	0		disp	0
C1	BNE	0	x	x	0	x	x		0	0	0	0	0	0	x	x	0		disp	0
C0	BEQ	0	x	x	0	x	x		0	0	0	0	0	0	x	x	0		disp	0
CE	B[AL]	0	x	x	0	x	x		0	0	0	0	0	0	x	x	0		disp	0
10000	JMP	0	x	x	0	x	x		0	0	0	0	0	0	x	x	0		instr[10:0]	1
10001	JAL	1	instr[10:8]	pcaddr	1	x	x		0	0	0	0	0	0	x	x	0		disp	0
10010	JAL	1	instr[10:8]	pcaddr	1	instr[7:5]		0x0000	1	0	0	0	0	0	x	x	0		ALUout	1
10011	JR	0	x	x	0	instr[7:5]		0x0000	1	0	0	0	0	0	x	x	0		ALUout	1
11100	OutR	0	x	x	0	instr[7:5]		0x0000	1	0	0	0	0	0	x	x	0		1	0
11100	HIT	0	x	x	0	x	x	0	0	0	0	0	0	0	x	x	1		0	0

設計部分，一開始選這堂課的時候，就知道這堂課
需要具備計算機組織與數位邏輯還有寫硬體描述語言


的能力，因此架構的部分除了上網查之外，也上了清大 OCW 的課程，所以在開始拉電路之前，資料該怎麼流與怎麼控制，已有初步的想法與規劃。

Schematic


1.16-Bit Complement Adder

 


2.LHI_LLI(用來處理 LHI 和 LLI 指令)

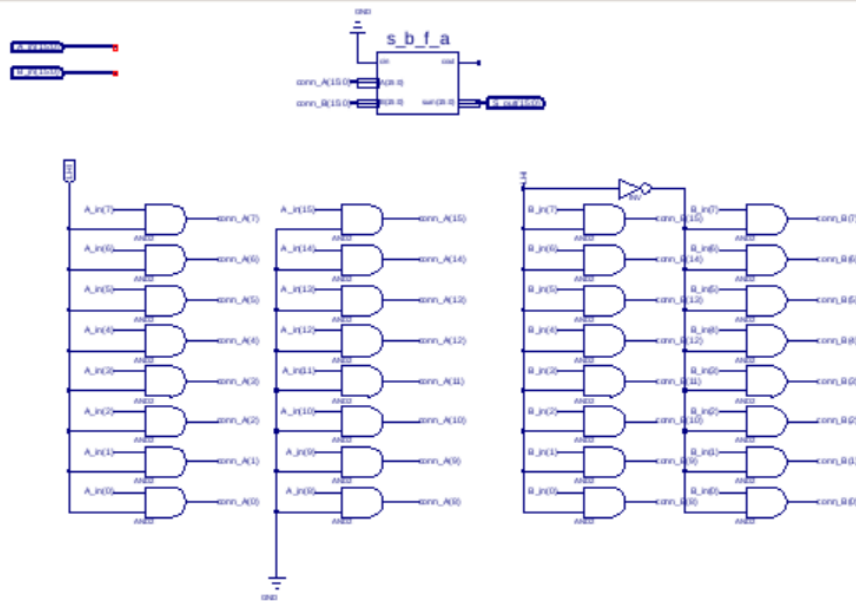


3.ALU

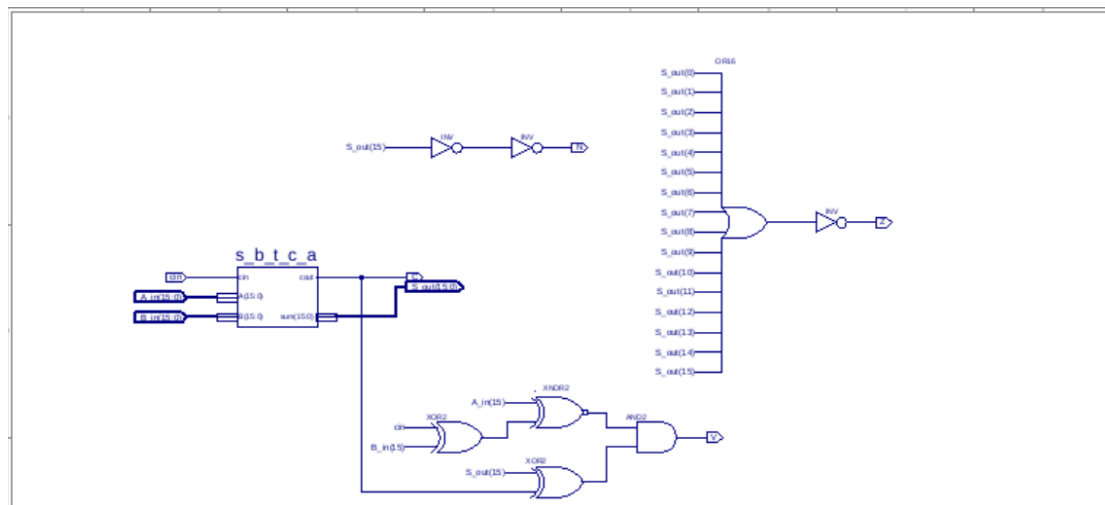


4.16-Bit Eight-Register Register File

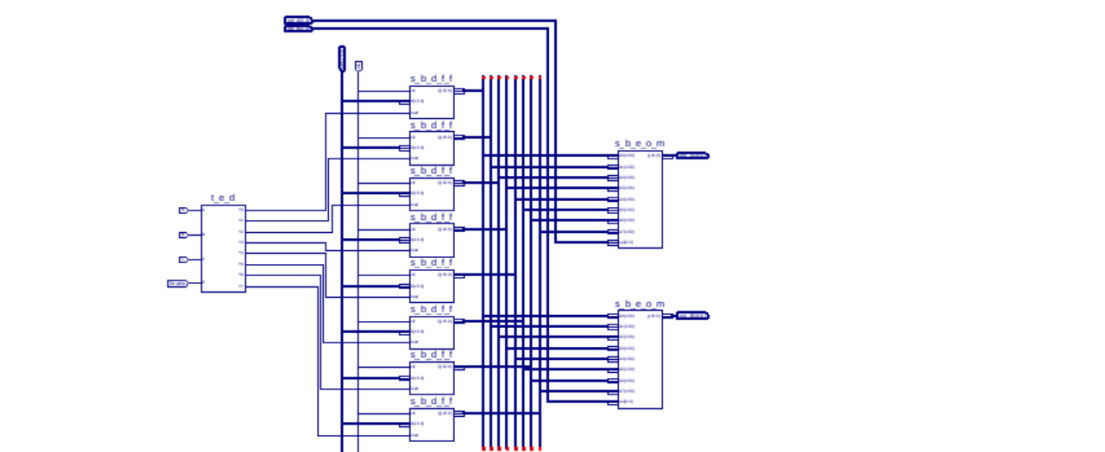


5.16-Bit RF-plus-ALU

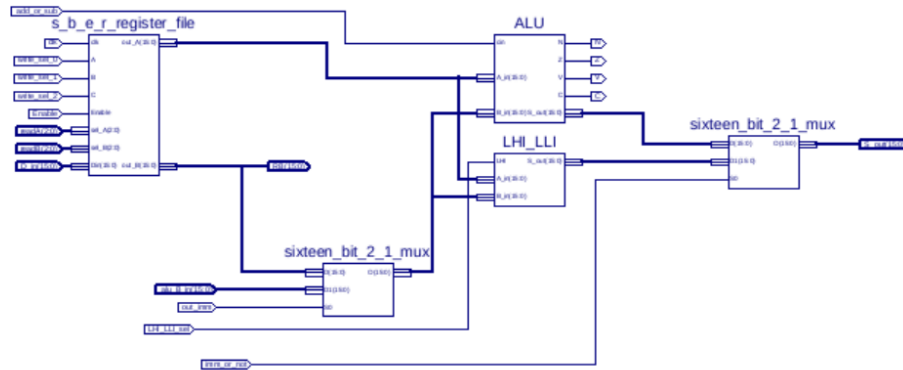


6.256*16 Memory Module

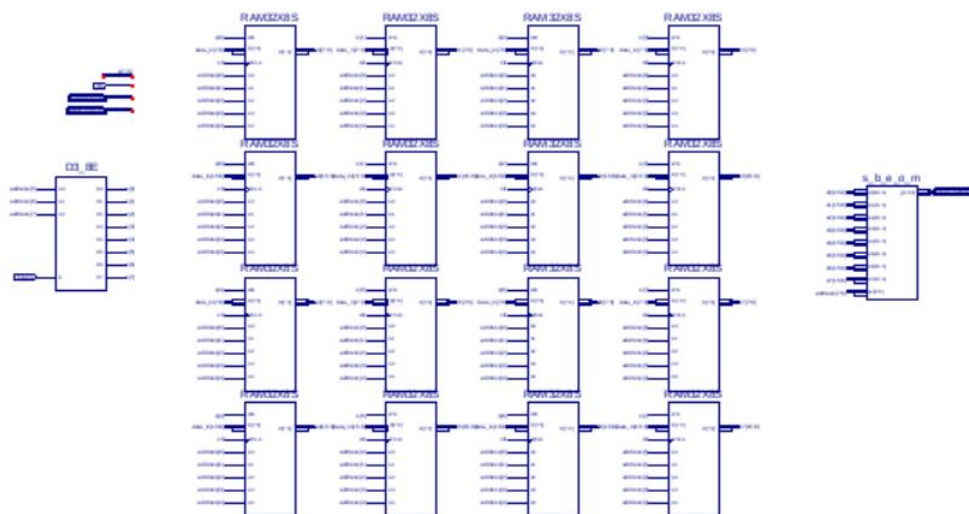


7.Program Counter

 


8.Instruction Decoder

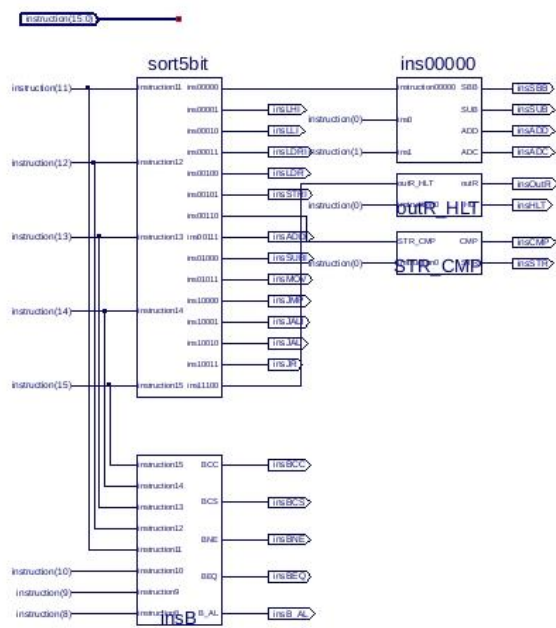


9.Datapath

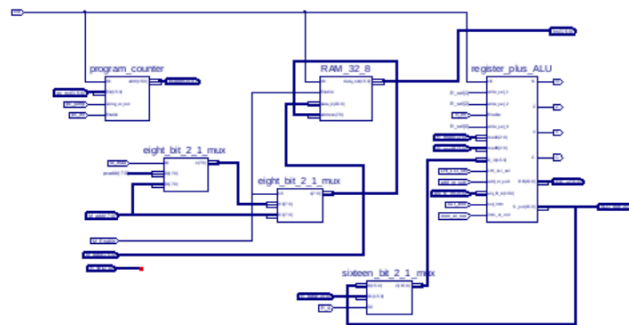

10.Controller(partial)

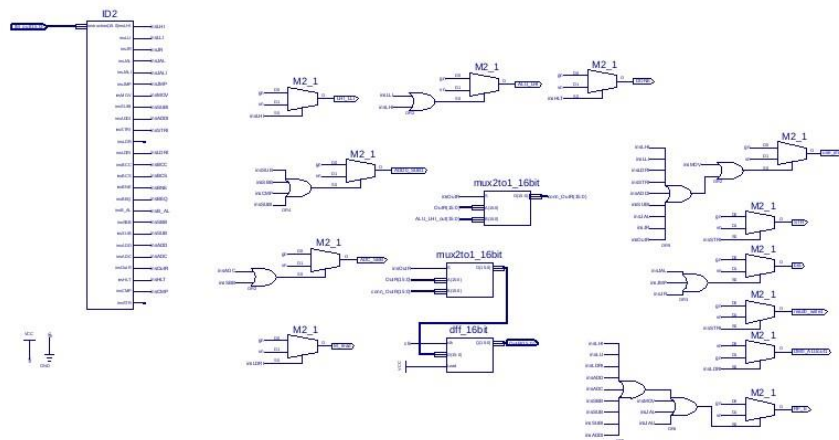


11.Complete Computer

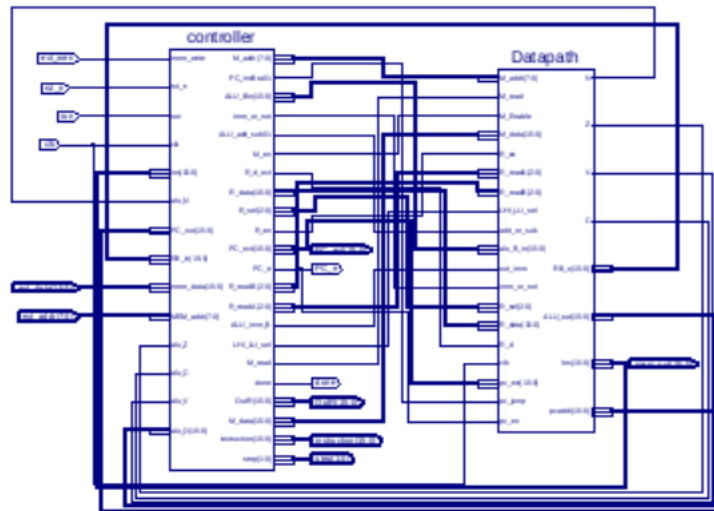


Verification

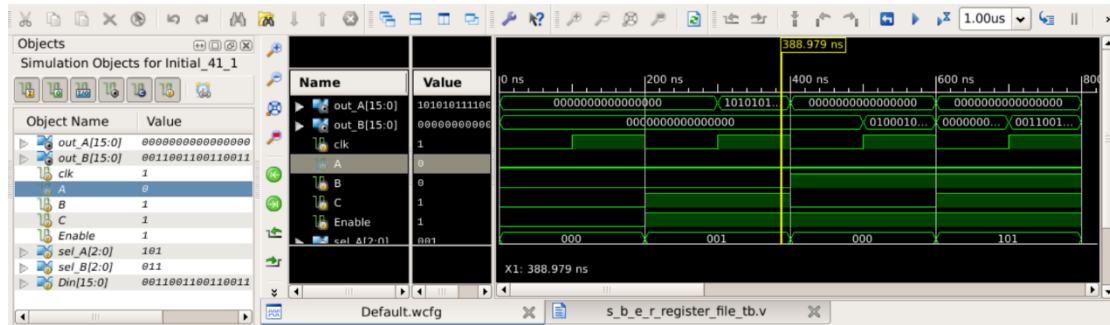1.16-Bit Eight-Register Register File Test Bench



Post-Route

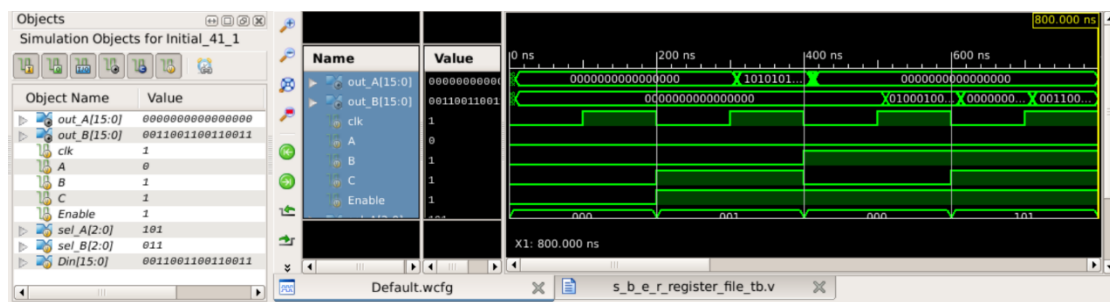

```

initial begin
    clk=0;
end
forever #100 clk=~clk;
initial begin
    A=0;
    B=0;
    C=0;
    Enable=0;
    sel_A[2:0]=0;
    sel_B[2:0]=0;
    Din[15:0]=0;
    #200;


    A=0;
    B=0;
    C=1;
    Enable=1;
    Din[15:0]=16'habcd;
    sel_A[2:0]=3'b001;
    sel_B[2:0]=3'b010;
    #200;

    A=0;
    B=1;
    C=0;
    Enable=1;
    Din[15:0]=16'h4444;
    sel_A[2:0]=3'b000;
    sel_B[2:0]=3'b010;
    #200;


    A=0;
    B=1;
    C=1;
    Enable=1;
    Din[15:0]=16'h3333;
    sel_A[2:0]=3'b101;
    sel_B[2:0]=3'b011;
    #200;

    $finish;
end
    
```

2.16-bit ALU Test Bench

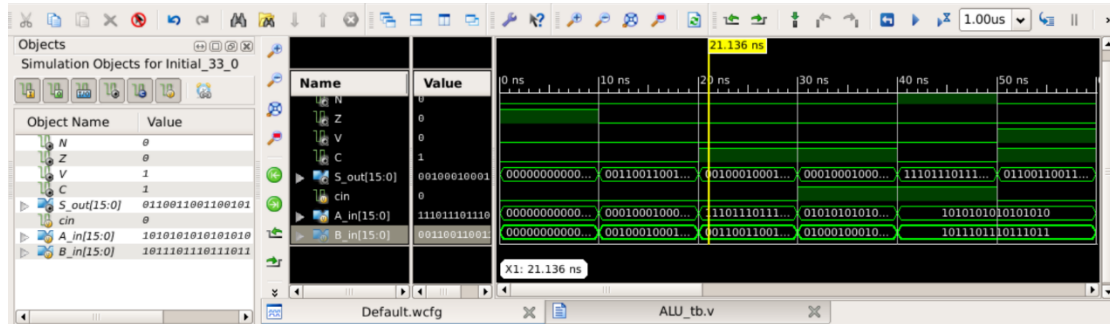

Post-Route

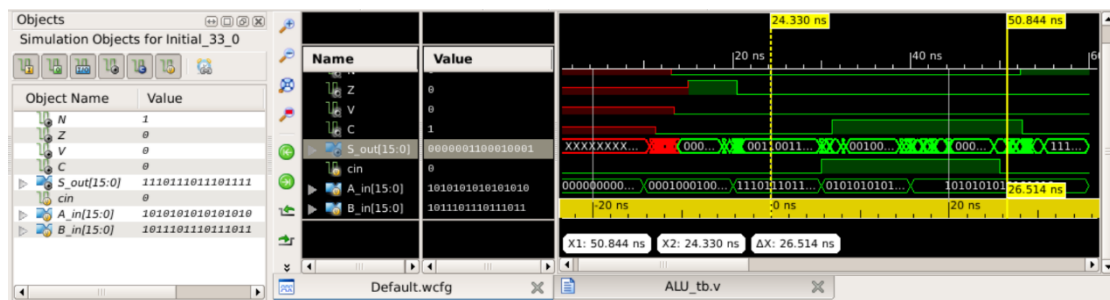

```

initial begin
    cin=0;
    A_in[15:0]=0;
    B_in[15:0]=0;
    #10;

    cin=0;
    A_in[15:0]=16'h1111;
    B_in[15:0]=16'h2222;
    #10;

    cin=0;
    A_in[15:0]=16'heeee;
    B_in[15:0]=16'h3333;
    #10;

    cin=1;
    A_in[15:0]=16'h5555;
    B_in[15:0]=16'h4444;
    #10;



    cin=1;
    A_in[15:0]=16'haaaa;
    B_in[15:0]=16'hbbbb;
    #10;

    cin=0;
    A_in[15:0]=16'haaaa;
    B_in[15:0]=16'hbbbb;
    #10;



end

```


3.16-Bit RF-plus-ALU Test Bench

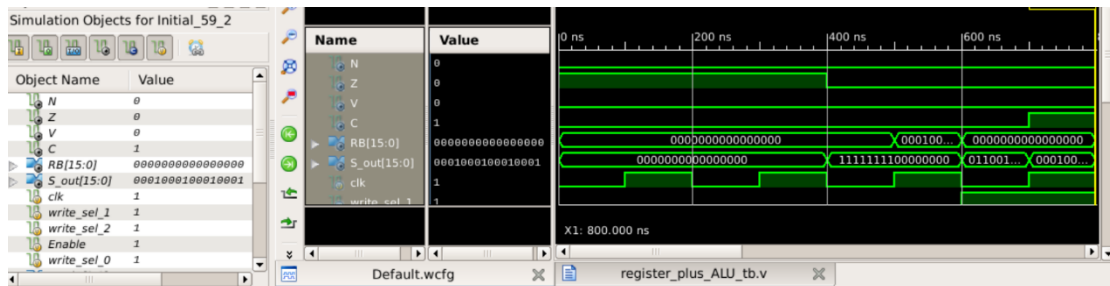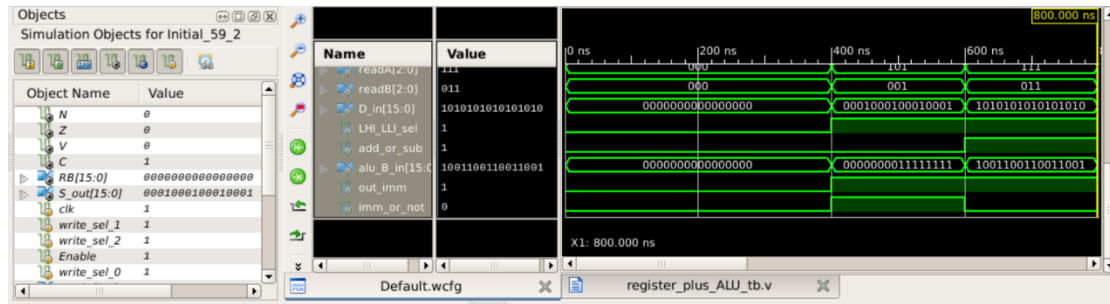


Post-Route

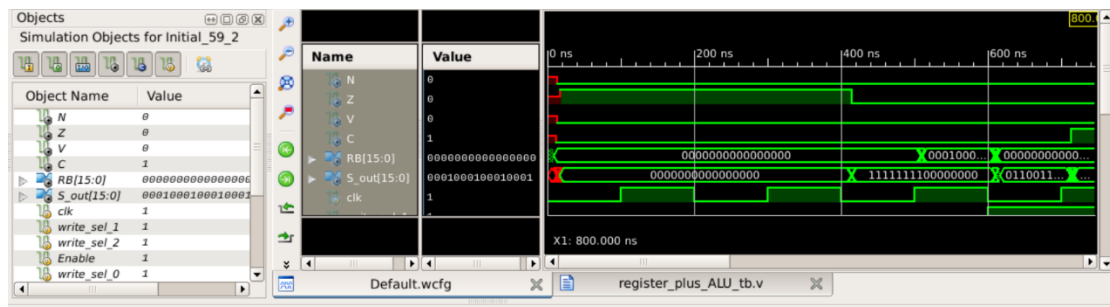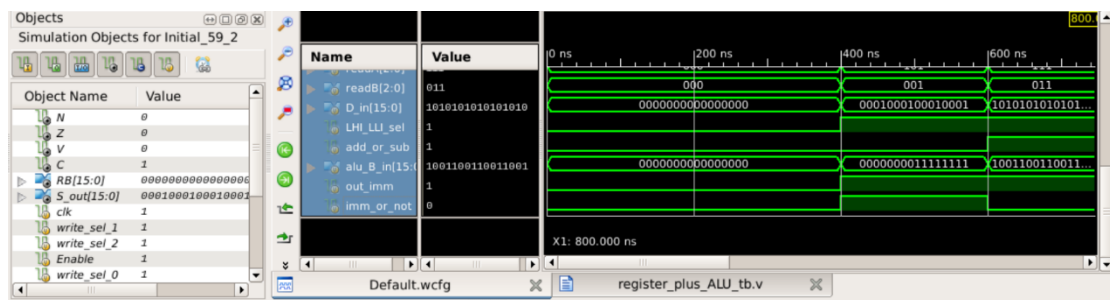


4.256*16 Memory Module Test Bench

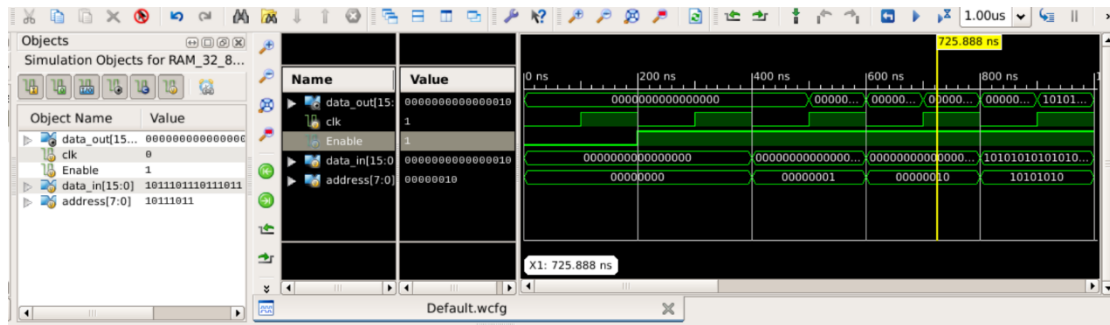


Post-Route

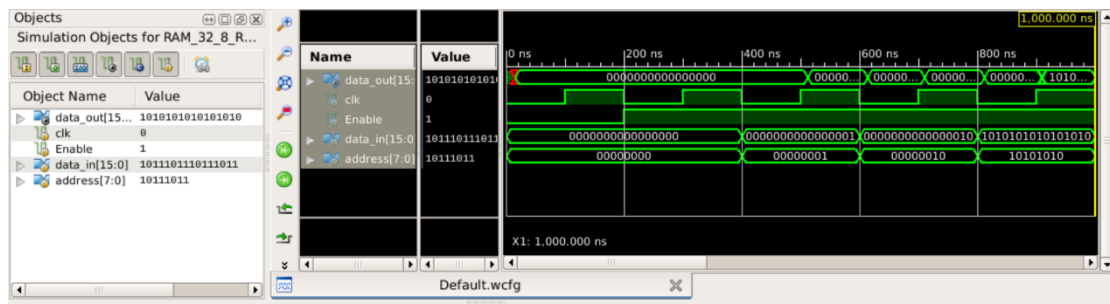

5.Program Counter Test Bench

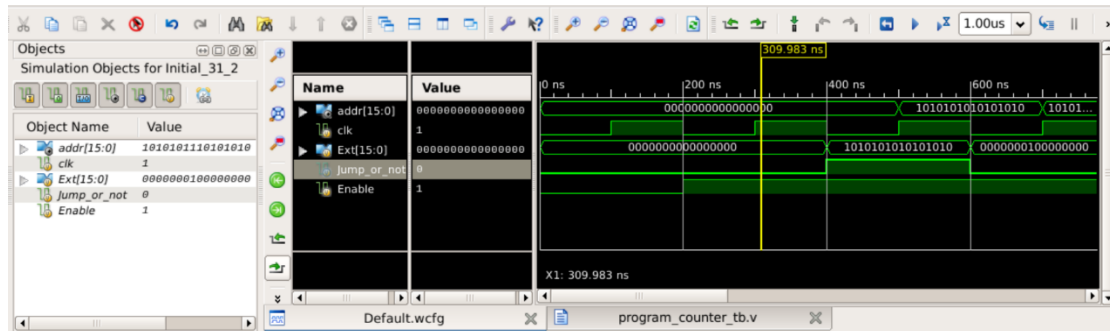

Post-Route

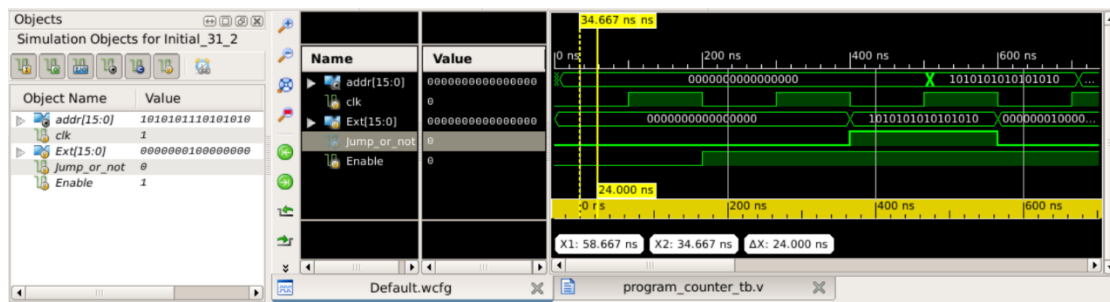


6.Controller Test Bench




Post-Route



7.Instruction Decoder Test Bench

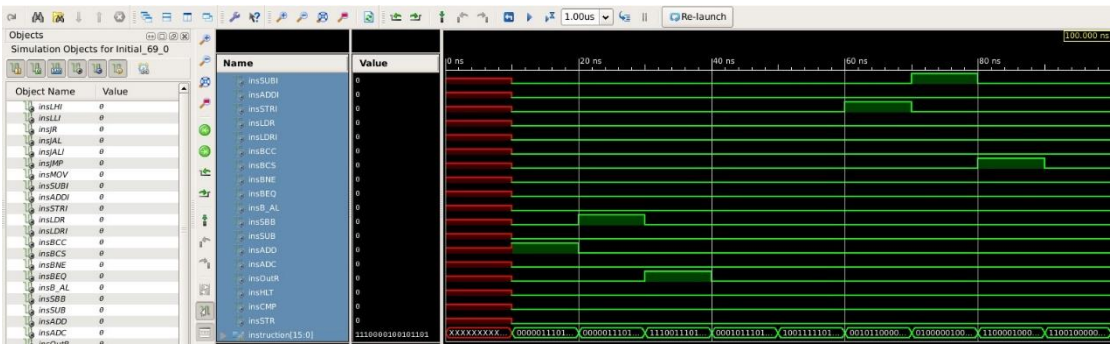

Post-Route

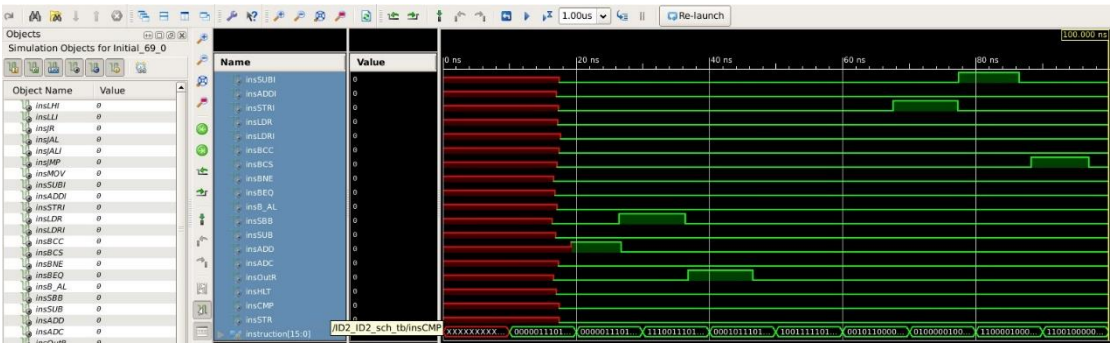


1. Find the minimum and maximum from two numbers in memory

	A	B	C	D
1	HEX	label	ASSEMBLY	COMMAND
2	0		LLI R0,#30H	00010_000_00110000
3	1		LLI R1,#37H	00010_001_00110111
4	2		LLI R2,#255	00010_010_11111111
5	3		LHI R2,#7fH	00001_010_01111111
6	4		LLI R3,#0	00010_011_00000000
7	5	lab0	LDR R4,R0,#0	00011_100_000_00000
8	6		CMP R2,R4	00110_000_010_100_01
9	7		BCC lab1	11000011_00000010
10	8		MOV R2,R4	01011_010_100_00000
11	9	lab1	CMP R3,R4	00110_000_011_100_01
12	a		BCS lab2	11000010_00000010
13	b		MOV R3,R4	01011_011_100_00000
14	c	lab2	ADDI R0,R0,#1	00111_000_000_00001
15	d		CMP R1,R0	00110_000_001_000_01
16	e		BNE lab0	11000001_11110111
17	f		OutR R2	11100_000_010_000_00
18	10		OutR R3	11100_000_011_000_00
19	11		HLT	11100_00000000_01

```


write_mem(16'h0,16'b00010_000_00110000 ) ;//LLI R0,#30H
write_mem(16'h1,16'b00010_001_00110111 ) ;//LLI R1,#37H
write_mem(16'h3,16'b00010_010_11111111 ) ;//LLI R2,#255
write_mem(16'h4,16'b00001_010_01111111 ) ;//LHI R2,#7fH
write_mem(16'h5,16'b00010_011_00000000 ) ;//LLI R3,#0
write_mem(16'h6,16'b00011_100_000_00000 ) ;//LDR R4,R0,#0
write_mem(16'h7,16'b00110_000_010_100_01 ) ;//CMP R2,R4
write_mem(16'h8,16'b11000011_00000010 ) ;//BCC lab1
write_mem(16'h9,16'b01011_010_100_00000 ) ;//MOV R2,R4
write_mem(16'hA,16'b00110_000_011_100_01 ) ;//CMP R3,R4
write_mem(16'hA,16'b11000010_00000010 ) ;//BCS lab2
write_mem(16'hB,16'b01011_011_100_00000 ) ;//MOV R3,R4
write_mem(16'hB,16'b00111_000_000_00001 ) ;//ADDI R0,R0,#1
write_mem(16'hB,16'b00110_000_001_000_01 ) ;//CMP R1,R0
write_mem(16'hB,16'b11000001_11110111 ) ;//BNE lab0
write_mem(16'hB,16'b11100_000_010_000_00 ) ;//OutR R2
write_mem(16'hB,16'b11100_000_011_000_00 ) ;//OutR R3
write_mem(16'hB,16'b11100_000000000_01 ) ;//HLT

```

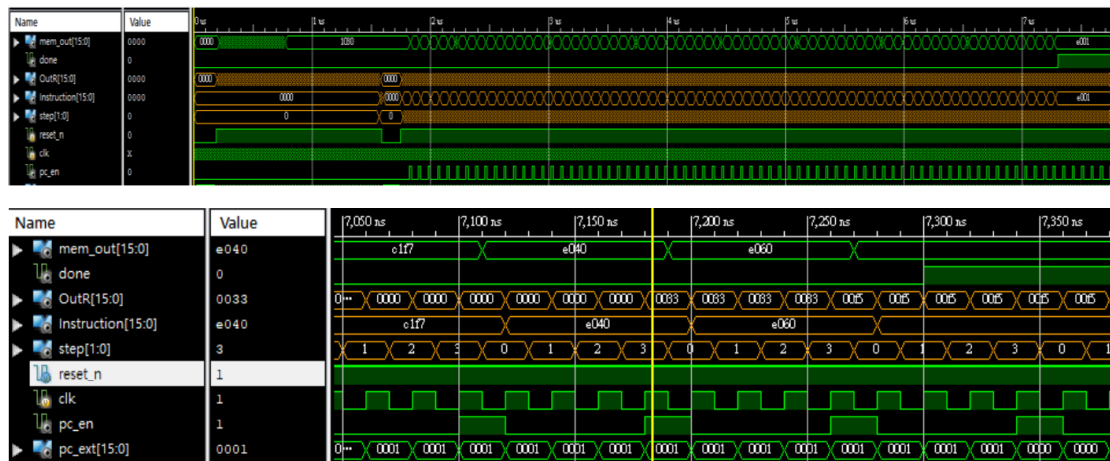

 2. Add two numbers in memory and store the result in memory location

```
write_mem(16'h0,16'b00010_000_00110000 ) ;//LLI R0,#30H
write_mem(16'h1,16'b00011_011_000_00000 ) ; //LDR R3,R0,#0
write_mem(16'h2,16'b00011_100_000_00001 ) ; //LDR R4,R0,#1
write_mem(16'h3,16'b00000_010_011_100_00 ) ; //ADD R2,R3,R4
write_mem(16'h4,16'b00101_010_000_00010 ) ; //STR R4,R0,#0
write_mem(16'h5,16'b00011_001_000_00010 ) ; //LDR R1,R0,#2
write_mem(16'h6,16'b11100_000_001_000_00 ) ; //OutR R1
write_mem(16'h7,16'b11100_000000000_01 ) ; //HLT
```




 3. Add ten numbers in consecutive memory locations

```
write_mem(16'h0,16'b00010_000_00110000 ) ;//LLI R0,#30H
write_mem(16'h1,16'b00010_010_00111001 ) ;//LLI R2,#39H
write_mem(16'h2,16'b00011_001_000_00000 ) ; //LDR R1,R0,#0
write_mem(16'h3,16'b00111_001_001_011_00 ) ; //ADDI R0,R0,#1
write_mem(16'h4,16'b00011_011_000_00000 ) ; //LDR R3,R0,#0
write_mem(16'h5,16'b00000_001_001_011_00 ) ; //ADD R1,R1,R3
write_mem(16'h6,16'b00110_000_010_000_01 ) ; //CMP R2,R0
write_mem(16'h7,16'b11000001_11110111 ) ; //BNE lab0
```



```
write_mem(16'h8,16'b11100_000_001_000_00 ); //OutR R1
write_mem(16'h9,16'b11100_000000000_01 ); //HLT
```




4. Mov a memory block of N words from one place to another

```

write_mem(16'h0,16'b00010_000_00110000 ) ;//LLI R0,#30H
write_mem(16'h1,16'b00010_010_00111001 ) ;//LLI R2,#39H
write_mem(16'h2,16'b00011_001_000_00000 ) ; //LDR R1,R0,#0
write_mem(16'h3,16'b00111_001_001_011_00 ) ; //ADDI R0,R0,#1
write_mem(16'h4,16'b00011_011_000_00000 ) ; //LDR R3,R0,#0
write_mem(16'h5,16'b00000_001_001_011_00 ) ; //ADD R1,R1,R3
write_mem(16'h6,16'b00110_000_010_000_01 ) ; //CMP R2,R0
write_mem(16'h7,16'b11000001_11110111 ) ; //BNE lab0
write_mem(16'h8,16'b11100_000_001_000_00 ) ; //OutR R1
write mem(16'h9,16'b11100 000000000 01 ) ; //HLT

```

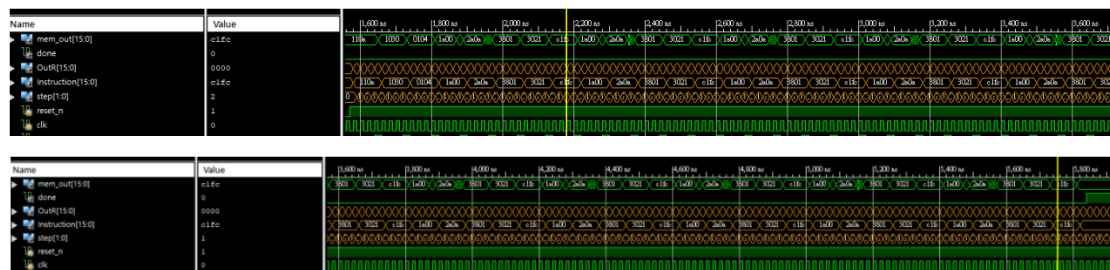

Hardware Cost

16-bits RISC CPU hardware cost

Device Utilization Summary			
Slice Logic Utilization	Used	Available	Utilization
Number of Slice Registers	136	30,064	1%
Number used as Flip Flops	136		
Number used as Latches	0		
Number used as Latch-thrus	0		
Number used as AND/OR logics	0		
Number of Slice LUTs	643	15,032	4%
Number used as logic	515	15,032	3%
Number using O6 output only	515		
Number using O5 output only	0		
Number using O5 and O6	0		
Number used as ROM	0		
Number used as Memory	128	3,664	3%
Number used as Dual Port RAM	0		
Number used as Single Port RAM	128		
Number using O6 output only	0		
Number using O5 output only	0		
Number using O5 and O6	128		
Number used as Shift Register	0		
Number of occupied Slices	220	3,758	5%

Total number of LUTs 643

Total number of FFs 136

Discussion

1. Design Entry

一開始我以為設計一個 RISC CPU 應該不難，因為網路上其實有很多類似的架構圖，但是再按圖施工的時候才發現，其實大部分有些東西都精簡過，所以如果沒先想好資料流動方式，其實是很容易卡關的。我花了很多時間在修改錯誤與理解每塊 **module** 的運作方式與功能，此外我大學的時候有學過數位邏輯和稍微寫過 **verilog**，但是電路是第一次拉，一開始蠻好玩的，可是遇到挫折的時候，其實蠻需要與人討論的，不然真的要花超多時間研究。最重要的地方是我認為我對每塊 **module** 的功能與溝通還不夠熟悉，**Term Project** 中也只有幾塊有很確切的解釋裡面該有哪些小模塊，其他就需要靠你對 **CPU** 架構的理解了。

2. Timing Simulation Error

另一方面就是我對時序的方面可能還不夠了解，我認為我的 **behavior simulation** 沒有太大的問題，但是在 **timing simulation** 上好像有些許錯誤，但是我可能無法如期找出問題把它修改好，接下來還要準備期中

考，希望我的期末 **Project** 可以把它改進並做得更好。