

FPGA System Designs and Practices (ET5009701)

Midterm Exam (Closed books and notes)

Date: December 1, 2021

Place: IB-410-1 and IB-410-2

Time limit: 120 minutes

This exam has seven problems in total. Please read each problem carefully and write your answers on the answer sheet.

1. (30%) Answer each of the following short questions:

- What are the two basic constructs (or blocks) used in the behavioral style?
- What are the three timing parameters you need to consider when using a flip-flop?
- Describe the meaning of the dataflow style.
- What is the meaning of the sampling window of a *D*-type flip-flop? What would happen when the sampling window is not satisfied?
- What are the three ways in Verilog HDL that can be used to define constants?

2. (10%) Explain and correct the following clock generator:

- Using both **always** and **initial** constructs

```
always begin
    initial clock = 1'b0;
    #5 clock = ~clock;
end
```

- Using the **always** construct

```
always begin
    #5 clock = ~clock;
end
```


$\{!a[4], !a[3], a[2:0]\}$
 $\{!a[4:3], a[2:0]\}$

3. (10%) Do the following two statements describe the same operations?

```
assign fifo_full = ({!gwr_ptr_next[n-1], !gwr_ptr_next[n-2],
                    gwr_ptr_next[n-3:0]} == grd_ptr);
assign fifo_full = ({!gwr_ptr_next[n-1:n-2],
                    gwr_ptr_next[n-3:0]} == grd_ptr);
```

 4. (20%) Assume that we want to describe a 3-to-1 multiplexer with the following interface:

```
module mux_3to1 (
    input i0, i1, i2 // inputs
    input [1:0] sel, // source selection inputs
    output out);    // output
// your answer is from here
.....
endmodule
```



case (sel)
 2'b00: out = i0;
 2'b01: out = i1;
 2'b11: out = i2;

Write a Verilog HDL module to describe this 3-to-1 multiplexer according to the ways specified as follows:

- (a) In behavioral style with a **case** statement
- (b) In behavioral style with an **if-else** statement
5. (20%) Consider a modulo-3 counter that generates one output pulse per three input pulses. Assume that the input pulse (*clk*) is a 50-% duty-cycle signal, and the output pulse (*qout*) must be also 50-% duty-cycle, as depicted in Figure 1.

 


Figure 1: Block diagram and waveform of Problem 5.

- (a) Design this modulo-3 counter and explain the rationale behind your design.
- (b) Plot the resulting logic diagram of the modulo-3 counter.
- (c) Write a Verilog HDL module to describe the resulting modulo-3 counter.
6. (10%) In this problem, you are asked to describe a register file with two read ports and one write port. The register file has the following features: The access to each read port is unconditional and asynchronous, and the access of the write port is controlled by a write enable signal, *wr_enable*, in synchronism with the clock (*clk*) signal. Each port regardless of read or write has its own access address.

```
// an N-word register file with one write port and two read ports
module register_file
    #(parameter M = 4, // default number of address bits
      parameter N = 16, // default number of words, N=2*M
      parameter W = 8) ( // default word width
      input clk, wr_enable,
      input [W-1:0] din, // data input
      input [M-1:0] rd_addra, rd_addrb, // read addresses
      input [M-1:0] wr_addr, // write address
      output [W-1:0] douta, doutb); // port_a and port_b outputs
    reg [W-1:0] reg_file [N-1:0];
    // your answer is from here
```

endmodule

7. (10%) Write a Verilog HDL module to describe a code converter that converts an excess-3 code to a BCD code. The code converter works as follows. It first checks to see whether the input codeword is a valid excess-3 code or not. If yes, it converts the input codeword into its equivalent BCD codeword by subtracting 4'b0011 from the input codeword and sets the valid signal true to indicate this situation; otherwise, it directly passes the input codeword to the output and sets the valid signal false.

```
module excess3_to_BCD(  
    input  [3:0] x, // excess-3 input  
    output [3:0] y, // BCD output  
    output valid); // indicate a valid excess-3 input  
// the body of the excess-3-to-BCD converter  
assign valid = // complete this assignment using the ?: operator  
assign y =     // complete this assignment using the ?: operator  
endmodule
```

—— End of exam ——